

Indian Institute of Technology, GUWAHATI

(A)

IIT, GUWAHATI

Table No. - 08 / Group No. - 08 / Lab group - 2-3(B)

EE 102: Basic → Electronics Laboratory.

Expt. No. 7 & 8 : Common Emitter Amplifier

Group Members

ROLL No.

Date :- 5<sup>th</sup>, April, 2019

Ankita Singh 180122008

Arpit Kumar Jain 18122009

Arinash Kodwate 180122010

Pre-Lab. - attached with this.-

# INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI

Department of Electronics & Electrical Engineering

EE102: Basic Electronics Laboratory

Expt.No. 7 & 8: Common Emitter Amplifier

## Objectives:

1. To carry out an approximate DC and AC analysis of the given CE amplifier.
2. To determine the voltage gain, the "maximum undistorted peak-to-peak output voltage swing" (MUOVS) and the maximum input voltage for undistorted output.
3. To study the effect of emitter bypass capacitor on voltage gain.

## Materials Required:

1. Equipment: Breadboard, Function Generator, Oscilloscope, Multi-Output Power Supply, Digital Multimeter.
2. Components: NPN type 2N2222A (One),  $470\Omega$  (One),  $1k\Omega$  (One),  $2.2k\Omega$  (One),  $22k\Omega$  (One),  $100k\Omega$  (One),  $10\mu F$  (Two),  $22\mu F$  (One),  $1k\Omega$  Pot (One)

## Precautions and Guidelines:

1. You are expected to come to the Lab with a neat report showing all calculations regarding the Pre Lab Work.
2. You will be allowed to perform the experiment only after the instructor has checked the report.

## Pre-Lab Work:

1. Carry out an approximate DC analysis by using the values given in Fig.1 and by making use of the assumptions  $I_{R1}, I_{R2} \gg I_B$ , so that  $I_{R1} \approx I_{R2}$  and  $V_{BE} \approx 0.65V$ . Estimate the DC quantities (quiescent values)  $V_B, V_E, V_C, I_E (\approx I_C)$ .
2. Draw the small signal equivalent of the circuit in Fig.1 and compute the voltage gain as  
$$Av = -(\beta \cdot R_C)/(r_b) \approx - (R_C)/(r_e) = - (R_C \cdot I_E)/(V_T) \approx - (R_C \cdot I_C)/(V_T)$$

Take  $V_T \approx 25mV$  (at room temp).
3. Compute MUOVS =  $2 \times \text{Min } \{V_{CC} - V_C, V_C - V_E\}$ .
4. How do you decide that the + terminal of  $C_1$  (an electrolytic capacitor) should be connected to the  $R_1-R_2$  node and the - terminal to the source  $v_i$ ? Likewise, for  $C_2$  and  $C_E$ .

## Part A: Measuring DC Quantities (Quiescent Values)

1. Before assembling the circuit, measure the actual values of the resistors by means of a Digital Multimeter (DMM). The actual values thus determined are to be used in calculating the currents.
2. Assemble the circuit, apply  $V_{CC}$  and note the following: (a) measure  $V_{BE}$  using a DMM and it should be around  $0.6V \sim 0.7V$  indicating that BE junction is forward biased. (b) Measure  $V_C$  and check if  $V_E < V_C < V_{CC}$ . A value of  $V_C$  midway between  $V_E$  and  $V_{CC}$  is preferable.

3. Measure  $V_B$ ,  $V_E$ ,  $V_C$  and  $V_{CC}$  and determine  $I_B$ ,  $I_E$ ,  $I_C$  and hence  $\beta$  ( $\beta = I_C/I_B$ ).  
 4. Compute  $A_v$  using the experimentally determined values of  $R_C$  and  $I_C$ . Use  $V_T = 25\text{mV}$ .

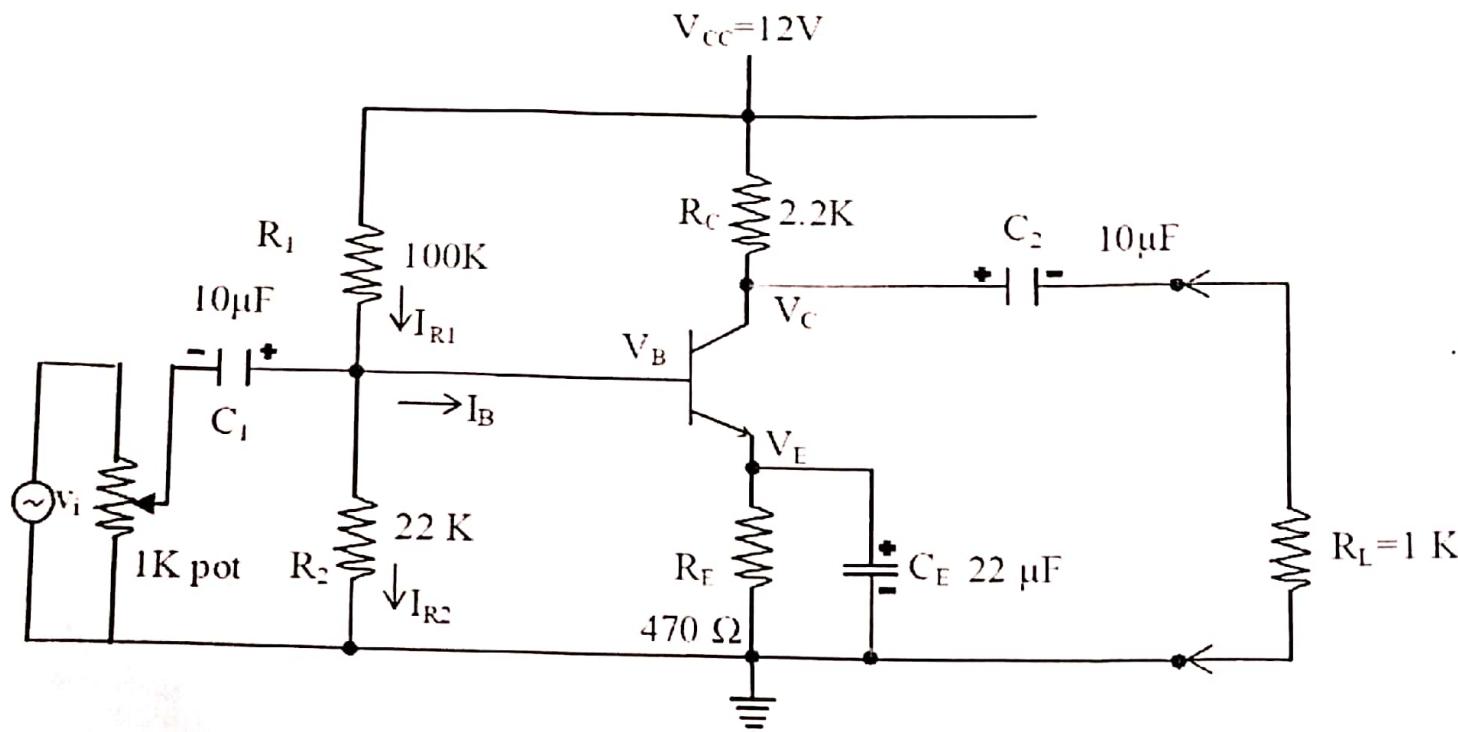


Fig. 1

#### Part B: Voltage Gain Without Load Resistance

1. Disconnect  $C_2$ . Adjust Function Generator to get approximately 10-20mV peak-to-peak sinusoid at 1kHz (display in Channel 1 of CRO). Apply this voltage at amplifier input  $V_i$ .
2. Display the collector voltage in Channel 2 of CRO (use DC coupling). Note the  $180^\circ$  phase difference between the input and the output.
3. Adjust  $V_i$ , p-p amplitude to get a convenient value for peak-to-peak collector voltage  $V_c$ , p-p (say 2V). Use appropriate vertical sensitivity (V/div). Note the corresponding  $V_i$ , p-p (mV).
4. Experimentally obtained voltage gain is therefore computed as:

$$A_v = - (V_c, \text{p-p}) / (V_i, \text{p-p}).$$

#### Part C: Maximum Undistorted Output Voltage Swing (MUOVS)

1. Increase  $V_i$ , p-p slowly till you observe a slight flattening of  $V_c$ , p-p waveform at its peaks (either positive peaks or negative peaks). The peak-to-peak value of the output signal (just at the onset of distortion/clipping) is the MUOVS. Measure the corresponding  $V_i$ , p-p, the peak-to-peak input voltage.
2. Now increase  $V_i$ , p-p beyond this point and observe the output waveform. The sinusoid gets increasingly flattened and becomes more like a square wave (overdriving an amplifier leads to heavy distortion).

#### Part D: Voltage Gain With Load Resistance

1. The output of an amplifier normally drives a load resistance  $R_L$  which may represent an actual load like an ear-phone or a loudspeaker, or the input impedance of another stage of the amplifier.

- ✓ 2. Connect  $R_L$  (see Fig.1) to the collector through the coupling capacitor  $C_2$  ( $C_2$  blocks the DC voltage at the collector and allows only the AC i.e. the signal component to pass through).
- ✓ 3. Measure  $A_v$  with  $R_L$  connected. (you would observe a reduced  $A_v$  since  $R_{C,\text{eff}} = R_C \parallel R_L$ .)

#### Part E: Effects of $C_E$ on $A_v$

- ✓ 1. Get back to the conditions in Part B i.e.  $V_I$  at 1 kHz, its amplitude adjusted to get  $V_{C,p-p} \approx 2V$ .
- ✓ 2. Now, remove  $C_E$  (with circuit powered) and note the drastic reduction in  $V_{C,p-p}$ . You have to change to appropriate V/div in your CRO. Determine the gain of the CE amplifier with unbypassed  $R_E$ .
- ✓ 3. Compare your observation with the theoretical value  

$$A_v = -\alpha R_C / (R_E + r_e) \approx -R_C / R_E$$
- ✓ 4. Display and sketch  $V_{I,p-p}$  and  $V_E$  waveforms. Note the amplitudes and the phase-relationship between them.
- ✓ 5. Display and sketch  $V_E$  and  $V_C$ . Note the amplitudes and the phase relationship. Please note that you are in DC coupling mode of the CRO. Please ensure that when you pressed the ground options in Channel 1 and Channel 2, both the horizontal traces (of the channels) are coinciding. Also ensure that the V/div of Channel 1 is equal to V/div of Channel 2.
- ✓ 6. Increase  $V_{I,p-p}$  gradually and observe how  $V_E$  and  $V_C$  change. Continue to increase  $V_{I,p-p}$  till you observe the +ve peak of  $V_E$  (almost) touching the negative peak of  $V_C$ . When this occurs, we say that the BJT has gone into saturation ( $V_{CE} \approx 0$ ).
- ✓ 7. What do you observe if  $V_{I,p-p}$  is increased beyond this point?


#### Part F: Lab Report

Prepare and submit a lab report as specified in the general instructions regarding the lab. Include the answers to the following questions in the report:

- ✓ 1. Why is  $V_C$  such that  $V_E < V_C < V_{CC}$  a preferred value in step 2 of Part A?
- ✓ 2. Compare the experimentally determined values of the currents and voltages in step 3 of part A with those you obtained through approximate analysis.
- ✓ 3. Compare the experimentally determined value of  $\beta$  in step 3 of part A with the approximate value given by the Lab Instructor.
- ✓ 4. Compare the experimentally determined value of the voltage gain  $A_v$  in step 4 of Part B with the computed values obtained in step 4 of Part A. Also compare this value with the value estimated in the Pre Lab Work.
- ✓ 5. What is the utility of knowing MUOVS in the design of an amplifier?

# RE-LAB WORK

1) The DC circuit is:

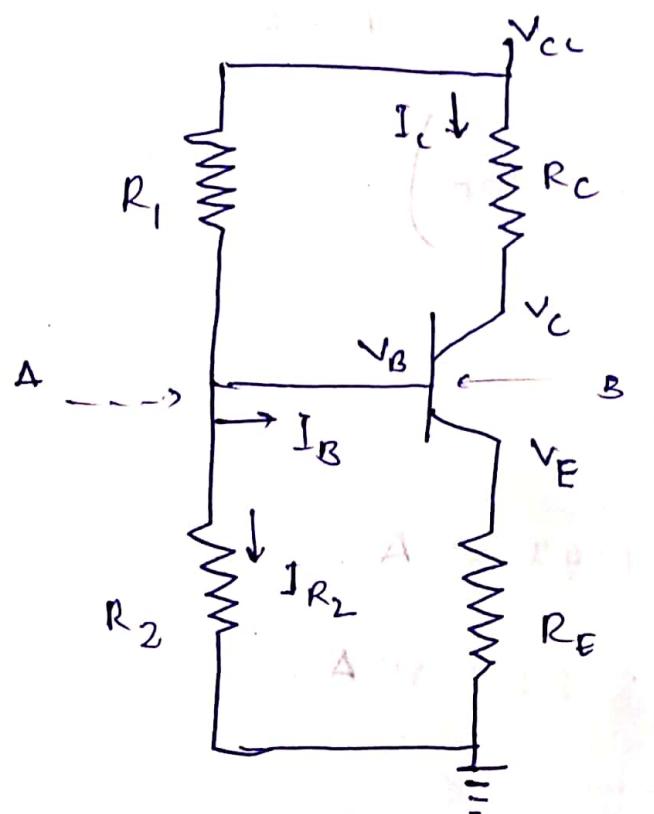

$$V_{CE} = 12 \text{ V}$$

$$R_1 = 100 \text{ k}\Omega$$

$$R_2 = 22 \text{ k}\Omega$$

$$R_C = 2.2 \text{ k}\Omega$$

$$R_E = 470 \text{ }\Omega$$

$$I_{R_1} \approx I_{R_2} \gg I_B$$

$$V_{B_1} \approx 0.65 \text{ V}$$

$$I_E \approx I_C$$

At point B

$$I_C + I_B = I_E$$

$$\text{Now } V_B = I_{R_2} R_2$$

$$V_C = V_{CC} - I_E R_C = V_{CC} - I_E R_C + I_B R_C$$

$$V_E = V_B - V_{BE} = I_E R_E$$

Using Kirchoff's Law

$$V_{CC} = I_{R_1} R_1 + I_{R_2} R_2 = I_{R_2} R_2 + (I_{R_2} + I_B) R_1$$

$$V_{CC} = I_E R_E + V_{BE} + (I_{R_2} + I_B) R_1$$

$$I_B = \frac{I_E}{B+1}$$

Applying given Approximations - of  $(\beta \rightarrow \infty, I_{R_1} \approx 0)$

$$V_{CC} = I_{R_2} (R_1 + R_2) \Rightarrow I_{R_2} = \frac{V_{CC}}{R_1 + R_2}$$

$$I_E = \frac{1}{R_E} \left( V_{CC} - \left( \frac{V_{CC}}{R_1 + R_2} \right) R_1 - V_{BE} \right)$$

$$= \frac{1}{R_E} \left( \frac{R_2}{R_1 + R_2} V_{CC} - V_{BE} \right)$$

Using values  $\Rightarrow I_{R_2} = 0.098 \text{ mA}$ .

$$I_E = 3.221 \text{ mA}$$

The voltages can now be calculated

$$V_B = I_{R_2} R_2 = \frac{R_2}{R_1 + R_2} V_{CC} \quad (1 = 0.098 \text{ mA})$$

With given Approx.  $I_E = I_C$  if  $I_B = 0$

$$V_C = V_{CC} - \frac{R_C}{R_E} \left[ \frac{R_2}{R_2 + R_1} V_{CC} - V_{BE} \right]$$

$$= \left[ 1 - \frac{R_C}{R_E} \cdot \frac{R_2}{R_2 + R_1} \right] V_{CC} + \frac{R_C}{R_E} V_{BE}$$

Putting values  $V_B = 2.164 \text{ V}$

$$V_C = (1.8709 + 3.0425) \text{ V}$$

$$V_C = 4.1938 \text{ V? } \quad \boxed{4.91}$$

$$\text{Also, } V_{BE} = V_B - V_E$$

$$V_E = V_B - V_{BE} = 2.164 \text{ V} - 0.65 \text{ V} = 1.514 \text{ V}$$


$$\text{Thus } V_B = 2.164 \text{ V}$$

$$V_E = 1.514 \text{ V}$$

$$V_C = 4.1938 \text{ V}$$

$$I_E = 3.221 \text{ mA}$$

2) small signal Equivalent circuit.

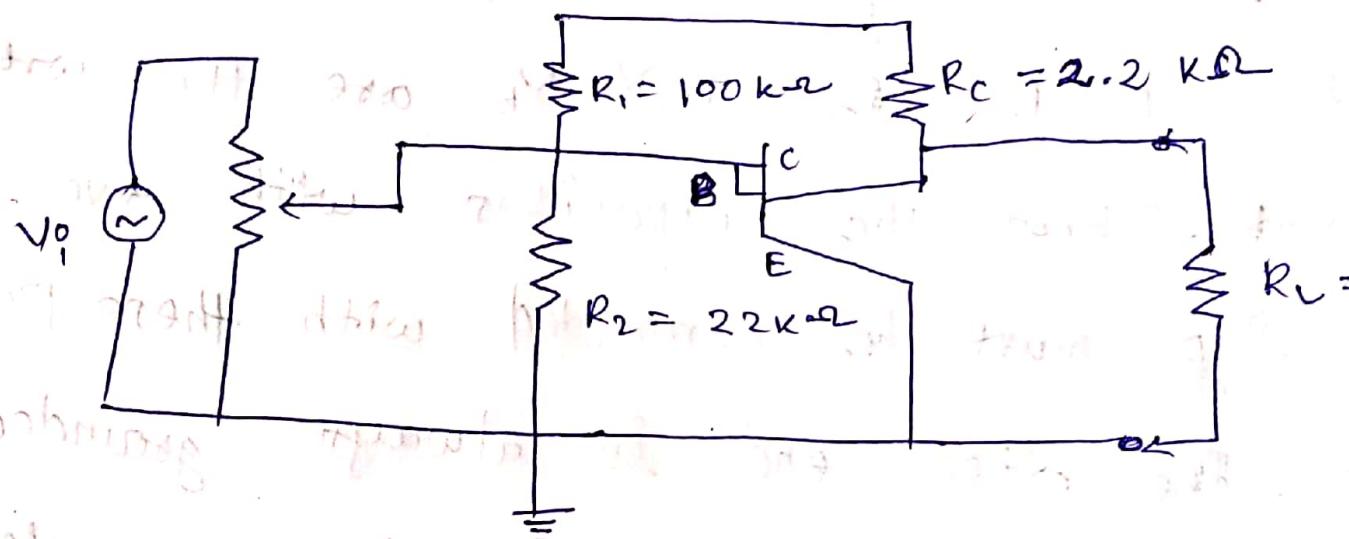

$$\text{Voltage gain, } A_v = -\frac{(R_C)}{\frac{r_b}{\beta_e}} = -\frac{(R_C)}{\frac{r_e}{\beta_e}} = -\frac{(R_C \cdot I_C)}{V_T}$$

$$= -\frac{(R_C \cdot I_C)}{V_T}$$

Where,  $V_T = 25 \text{ mV}$  (Thermal voltage at R.T)

$$I_C = I_E = 3.221 \text{ mA} \text{ (Quiescent values)}$$

$$R_C = 2.2 \text{ k}\Omega \text{ (given)}$$

$$\text{Thus } A_v = -\frac{2.2 \text{ k}\Omega \times 3.22 \text{ mA}}{25 \text{ mV}}$$

$$A_v \approx 283.448$$

3) Given  $MV_{OVS} = 2 \times \min(V_{CC} - V_C, V_C - V_E)$

Using Quiescent Values:

$$V_{CC} - V_C = (12 - 4.1938)V = 7.8062V$$

$$V_C - V_E = (\underline{4.1938} - \underline{1.514})V = \underline{\underline{2.6798}}V$$

Thus  $MV_{OVS} = 2 \times 2.6798V$   
 $= 5.3596V$

- 4) While performing DC analysis, the voltages of points B, C, E, i.e.,  $V_B, V_C, V_E$  are the wrt ground. Thus the capacitors with +ve polarity must be connected with these points, as the other end is always grounded, -ve of polarity can be safely connected to the opposite ends.

✓  
Date: 05/01/2019

## Measuring DC Quantities (Quiescent Values)

1.)	<u>Approx values</u>	<u>Real Values (DMM)</u>	<u>Digital Multimeter</u>
	470 $\Omega$	454 $\Omega$	
	1k $\Omega$	0.97k $\Omega$	
	2.2k $\Omega$	2.12k $\Omega$	
	22k $\Omega$	21.6k $\Omega$	
	100k $\Omega$	98.3k $\Omega$	

2.) (a)  $V_{cc} = 11.95V$

$$V_{BE} = V_B - V_E = 0.642V \text{ (forward bias)}$$

(b)  $V_C = 5.93V$

$$V_E = 1.278V$$

$$V_B = 1.916V$$

$\Rightarrow V_E < V_C < V_{cc}$

3.)  $V_B = 1.916V ;$

$$V_E = 1.278V ;$$

$$V_C = 5.93V ;$$

$$V_{cc} = 11.95V ;$$

$$I_E = \frac{V_E}{R_E} = \frac{1.278}{454} = 2.812 \text{ mA}$$

$$I_{R_1} = \frac{V_{cc} - V_B}{98.3} = \frac{11.95 - 1.916}{98.3} = 0.102 \text{ mA}$$

$$I_C = \frac{V_{cc} - V_C}{2.12} = \frac{11.95 - 5.93}{2.12} = 2.839 \text{ mA}$$

$$I_{R_2} = \frac{V_B}{21.6} = \frac{1.916}{21.6} = 0.088 \text{ mA}$$

$$I_B = I_{R_1} - I_{R_2} = 0.102 - 0.089 = 0.013 \text{ mA}$$

$$3) \beta = \frac{I_C}{I_B} = \frac{2.839}{0.013} = 218.38$$

$$4) A_v = -\frac{R_C I_C}{V_T}$$

$$V_T = 25 \text{ mV}; R_C = 212 \text{ k}\Omega; I_C = 2.839 \text{ mA}$$

$$A_v = -\frac{2.12 \times 2.839 \times 10^3}{25} = -240.75$$

Part B : Voltage Gain Without Load Resistance :-

After Disconnecting  $C_2$  :- 1) frequency  $\Rightarrow 1 \text{ kHz}$ . set approximately  $\Rightarrow 15 \text{ mV}$ .

$$V_{C, p-p} = 2 \text{ V}$$

$$\begin{aligned} \text{Multiplier 1} &\rightarrow \text{input} = 10 \text{ mV} \\ \text{Multiplier 2} &\rightarrow \text{output} = 1 \text{ V} \end{aligned}$$

$$3) V_i, p-p (\text{mV}) = 17 \text{ mV}$$

$$[\text{Time scale} = 0.5 \text{ ms}]$$

$$4) A_v = -\frac{(V_{C, p-p})}{(V_i, p-p)} = -\frac{2}{17 \text{ mV}} = 117.64$$

2)  $\rightarrow$  graph.

## :- Maximum Undistorted Output Voltage Swing (MUOVs)

Peak-to-Peak Input voltage:-

$$V_{i(p-p)} = 1.5 \times 50 = 75 \text{ mV} \quad (\text{Multiplier} = 50 \text{ mV})$$

Corresponding,  $V_{c(p-p)} = 8.3 \text{ V}$

For  $180^\circ$  output graph

Multplier → input = 50mV  
 Multplier → output = 5V  
 graph → .

Part D :- Voltage gain with load Resistance:-

$$R_L = 0.97 \text{ k}\Omega$$

$$R_C = 2.12 \text{ k}\Omega$$

$$V_{i(p-p)} = 45 \text{ mV}$$

$$R_C \text{ become } \rightarrow R_{C(\text{eff})} = R_C \parallel R_L$$

$$V_{c(p-p)} = 2 \text{ V}$$

$$R_{C(\text{eff})} = \frac{R_C \cdot R_L}{R_C + R_L}$$

$$A_V = -\left(\frac{-2}{45 \text{ mV}}\right) = 44.44 \rightarrow \text{reduced } A_V.$$

Part E :- Effects of  $C_E$  On  $A_V$  ⇒

$$1) V_{c(p-p)} \approx 2 \text{ V}$$

$1 \text{ kHz} = \text{frequency.}$  2) Remove  $C_E$

$$3) V_{i(-pp)} = 3.2 \times 50 \text{ mV} = 160 \text{ mV} \quad V_{c(-pp)} = 3.5 \times 0.2 \text{ V} = 0.7 \text{ V} = 700 \text{ mV.}$$

$$4) V_{i(p-p)} = 152 \text{ mV}$$

$$V_E(p-p) = -7.4 \times 20 = 148 \text{ mV}$$

→ graph

$$A_V = -\frac{700}{160} = 4.375.$$

$$A_{V,\text{theoretical}} = -\frac{R_C}{R_C} = \frac{2.12 \text{ k}\Omega}{454 \text{ }\Omega} = 4.67$$

→ Both have same phase.

5)

5.

Multiplier = 0.1

$$V_E = 1.6 \times 0.1 = 0.16 V$$

$$V_C = 7 \times 0.1 = 0.7 V$$

$V_E$  and  $V_C$  are  $180^\circ$  out of phase.

6.

On further increasing of  $V_1$  (P-P),  $V_E$  becomes square wave form both sides.

At touch (-ve & +ve)

$$V_C = 3.8 \times 2 = 7.6 V$$

$$V_E = 3.2 \times 0.5 = 1.6 V \quad 2 \times 1 = 2 V$$

∴ observed 1.6 V output.

At about  $V_E = 3.2 V$  (modulation voltage)  $V_E$  becomes zero.

∴  $V_C = 3.8 \times 0.5 = 1.9 V$  (modulation voltage)

∴  $V_E = 3.2 \times 0.5 = 1.6 V$  (modulation voltage)

∴  $V_C = 3.8 \times 0.5 = 1.9 V$  (modulation voltage)

∴  $V_E = 3.2 \times 0.5 = 1.6 V$  (modulation voltage)

∴  $V_C = 3.8 \times 0.5 = 1.9 V$  (modulation voltage)

Scale :- x-axis - time axis

1 unit = 0.5 sec/div.

$$f = 1 \text{ kHz}$$

$$T = 1 \text{ ms}$$


y axis - voltage axis

$$1 \text{ unit} = 1 \text{ V} \rightarrow \text{for output}$$

$$\therefore \text{multiplier} = 1 \text{ V}$$

$$1 \text{ unit} = 10 \text{ mV} \rightarrow \text{for input}$$
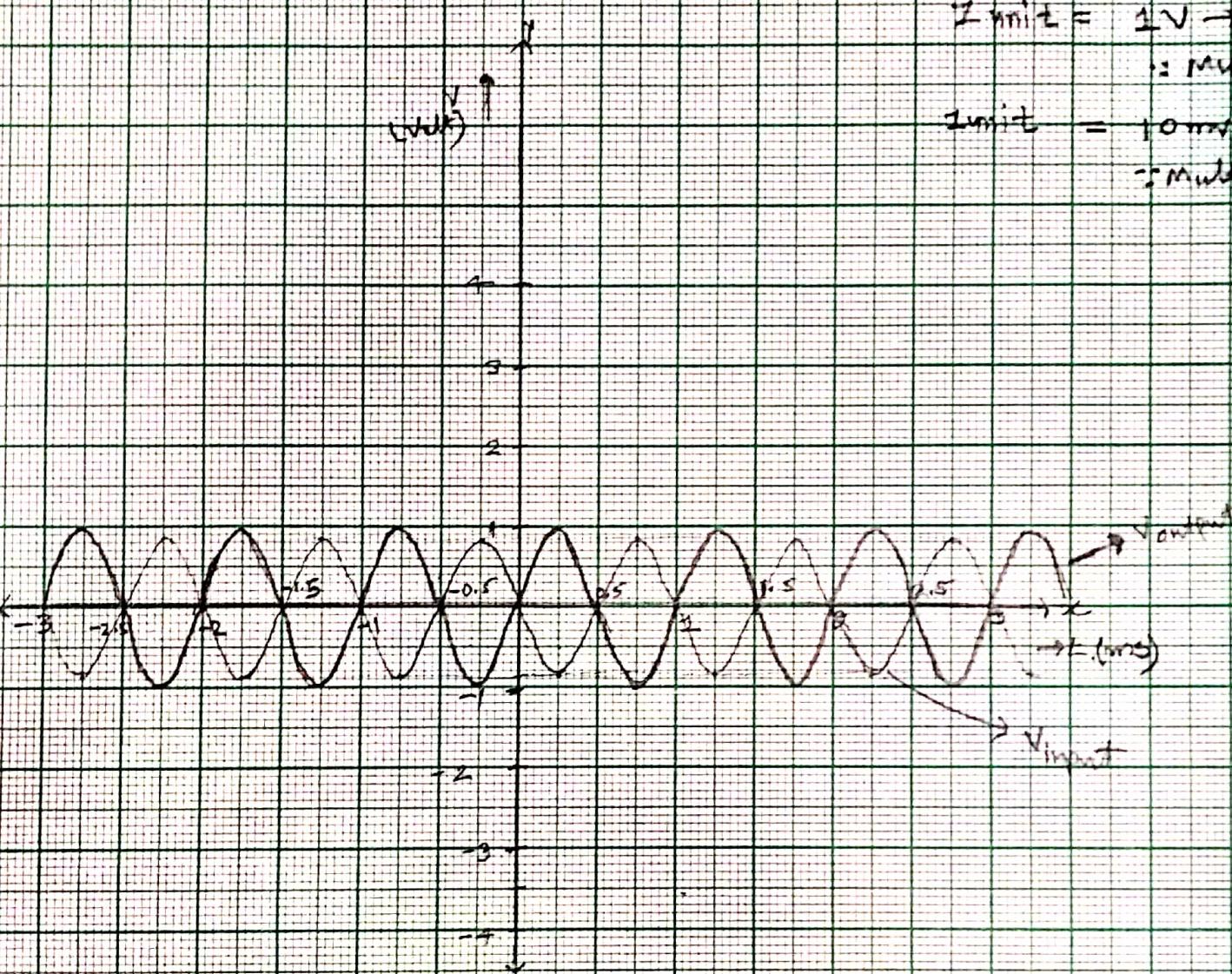
$$\therefore \text{multiplier} = 10 \text{ mV}$$



$$V_{\text{output P-P}} = 2 \times 2 \text{ V} = 4 \text{ V}$$

We observed 180°

phase difference

$$V_{\text{input}} = 2.7 + 1 \text{ (DC bias)} = 3.7 \text{ mV}$$

$$\text{Collector Voltage} \Rightarrow V_C = 2 \text{ V}$$

$$\text{input } V_{\text{P-P}} = 17 \text{ mV}$$

Part C - Point ① ⇒

Assignment

Page No.

Date 12/10/2019

Slight flattening of  $V_{C-pp}$

Scale -  $\rightarrow$  x-axis - Time axis


1 unit = 0.5 msec

y-axis → Voltage axis.

1 unit = 50 mV

$$V_{input} = 50 \times 1.5$$

$$= 75 \text{ mV.}$$

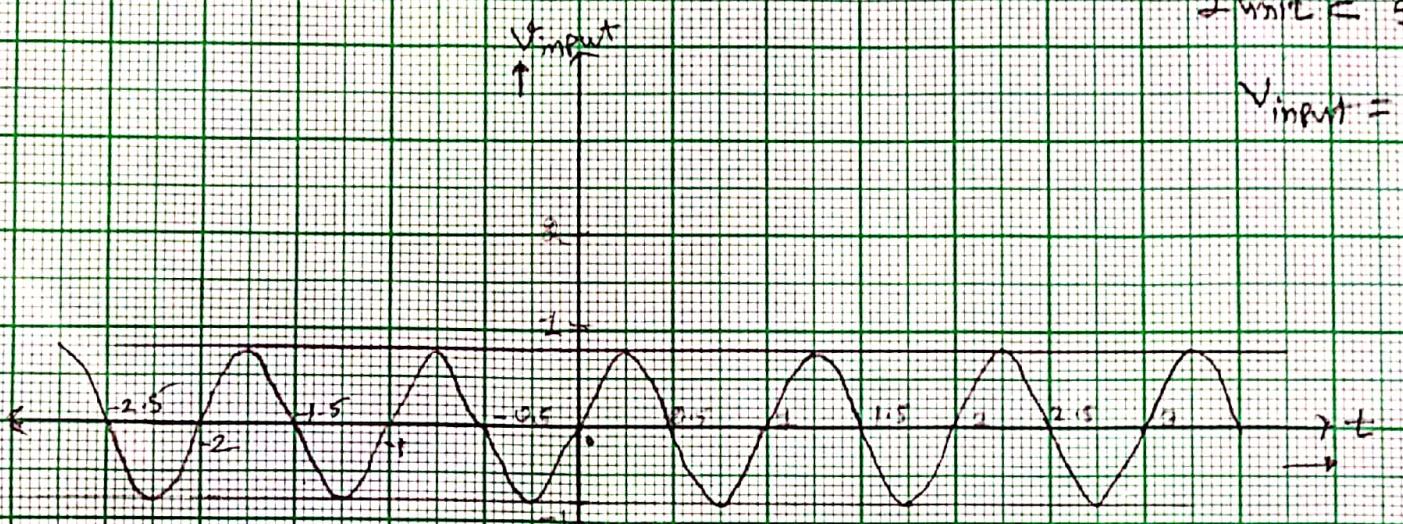


Scale - x-axis

1 unit = 0.5 msec

y-axis

1 unit = 5 V
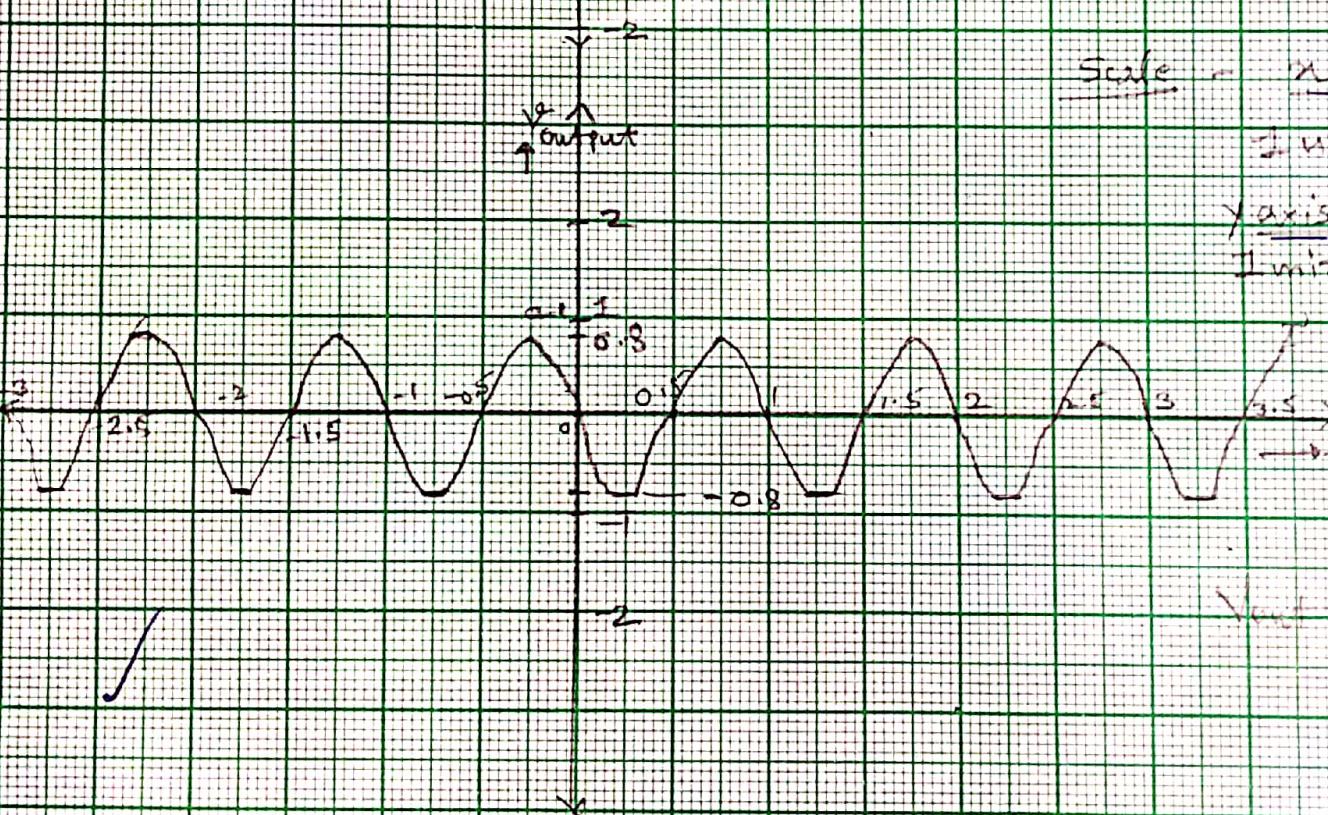
$$V_{output} = 5 \times 1.66 = 8.3 \text{ V}$$



We observed 180° out of Phase

Collector Voltage  $\Rightarrow V_C = 8.3 \text{ V}$

input  $\rightarrow V_{pp} = 75 \text{ mV.}$


Part - (E) Point (4)

graph between -  $V_E$  and  $V_{I-P-P}$ :

Scale -

x-axis time axis  
1 unit = 0.5 ms

y-axis - Voltage axis  
1 unit = 50 mV.

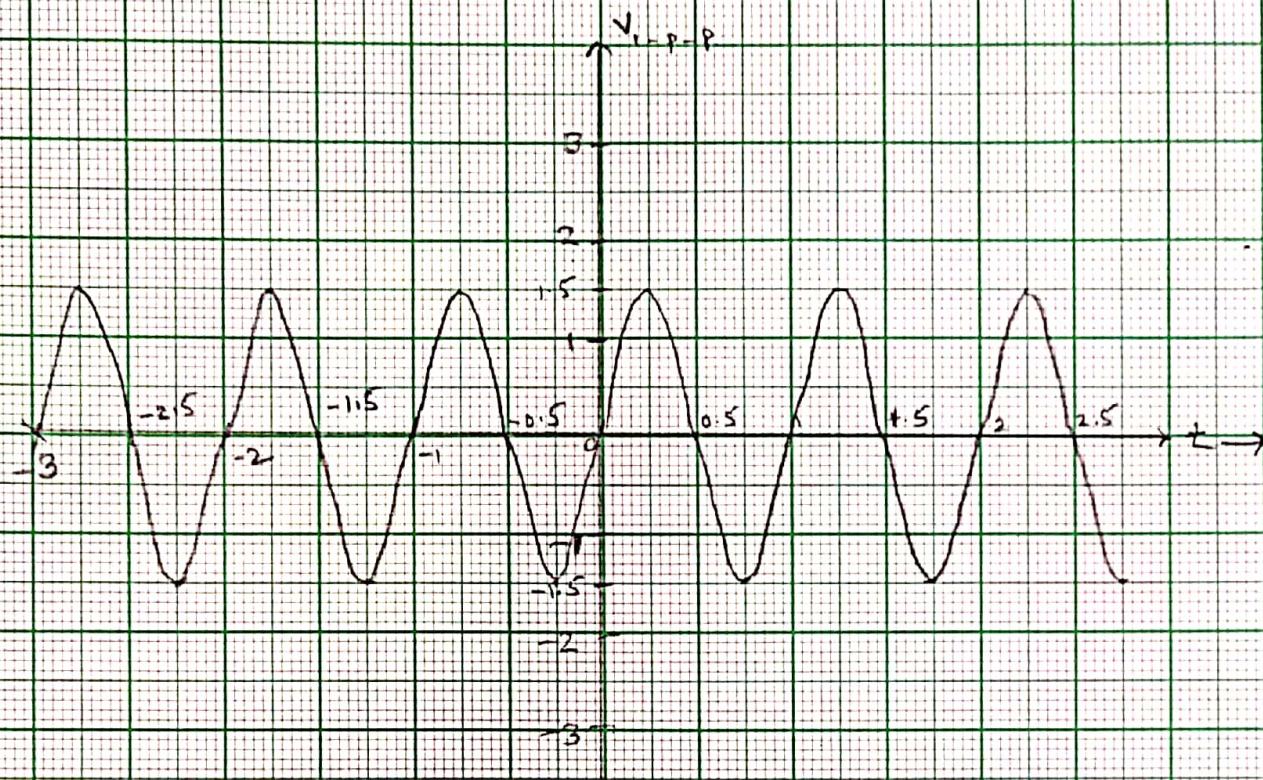


x axis : time scale

1 unit = 0.5 ms

y axis - voltage axis

1 unit = 50 mV

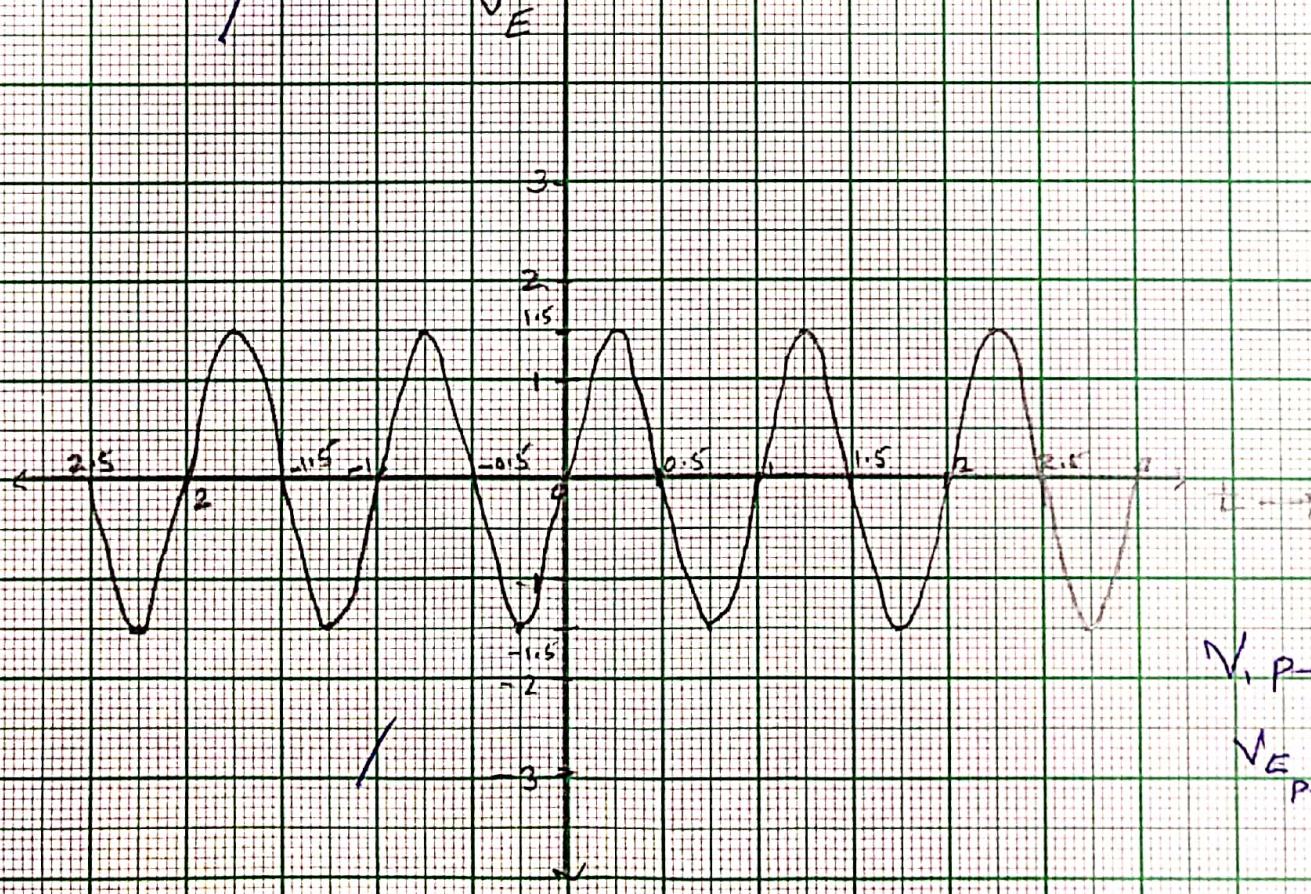

$$V_{I-P-P} = 152 \text{ mV}$$

$$V_E = 148 \text{ mV.}$$

We observed some phase

Part (E) Part (S) :-

graph between  $V_E$  and  $V_C$  :-

Scale


x-axis

time axis

1 unit = 0.5 ms

Y-axis - voltage axis

1 unit  $\Rightarrow$  0.2 Volt.

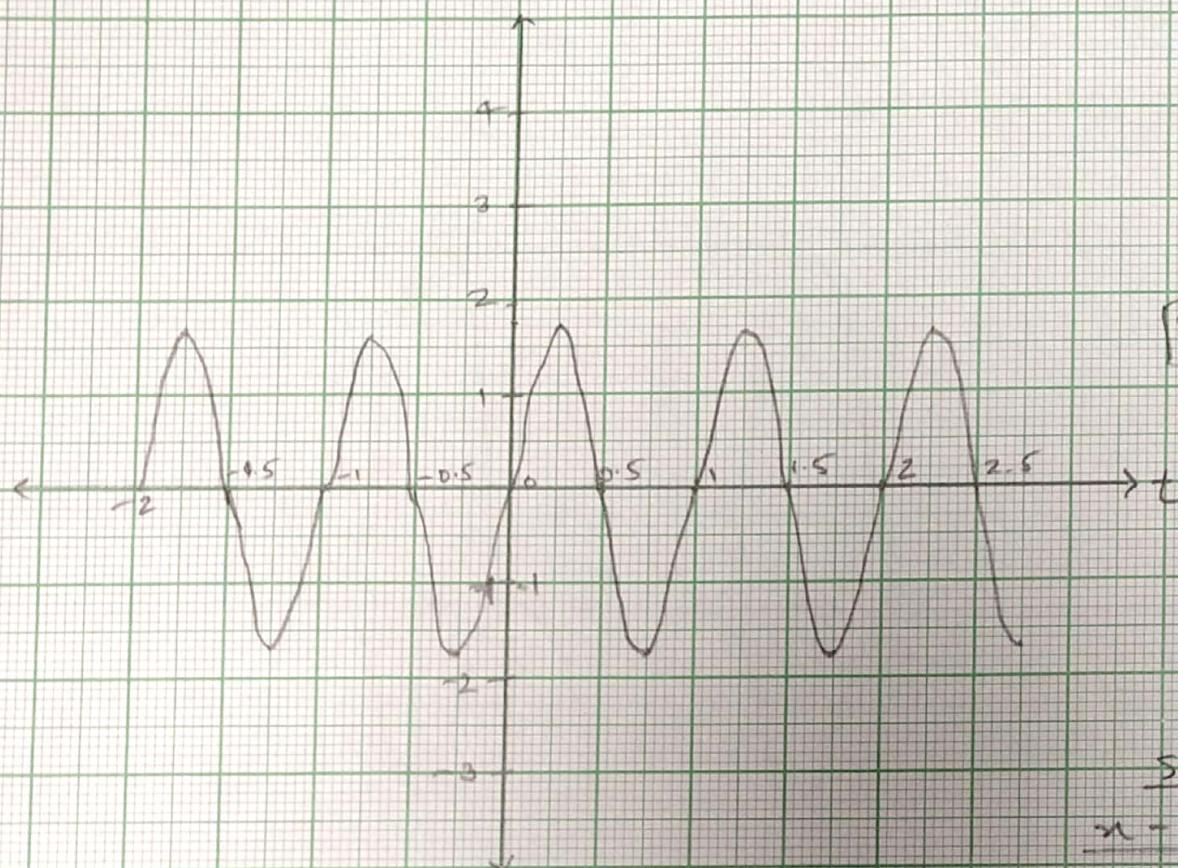

$$V_C = 3.5 \times 0.2 = 0.7 \text{ Volt.}$$

Scale


x-axis time axis

1 unit = 0.5 ms


Y-axis - voltage axis

1 unit = 0.1 Volt
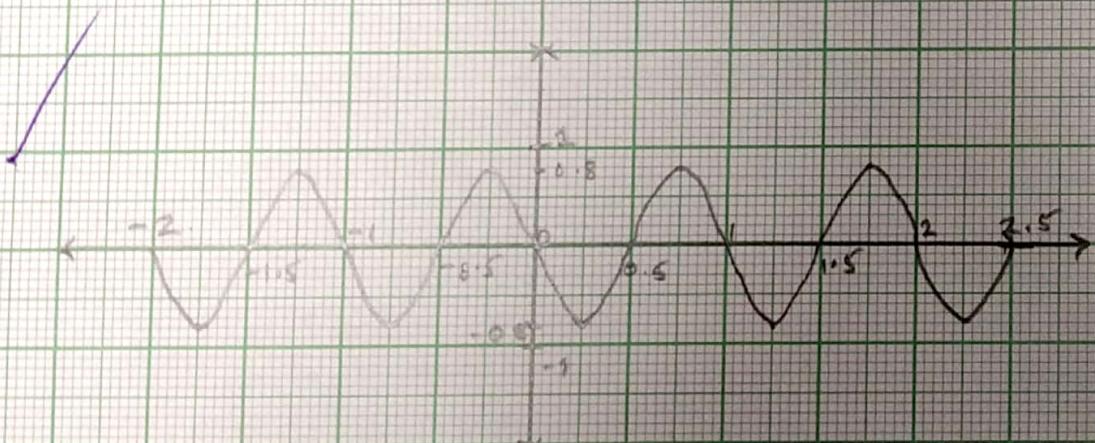
$$V_E = 1.6 \times 0.1 = 0.16 \text{ V}$$



We observed out of phase.

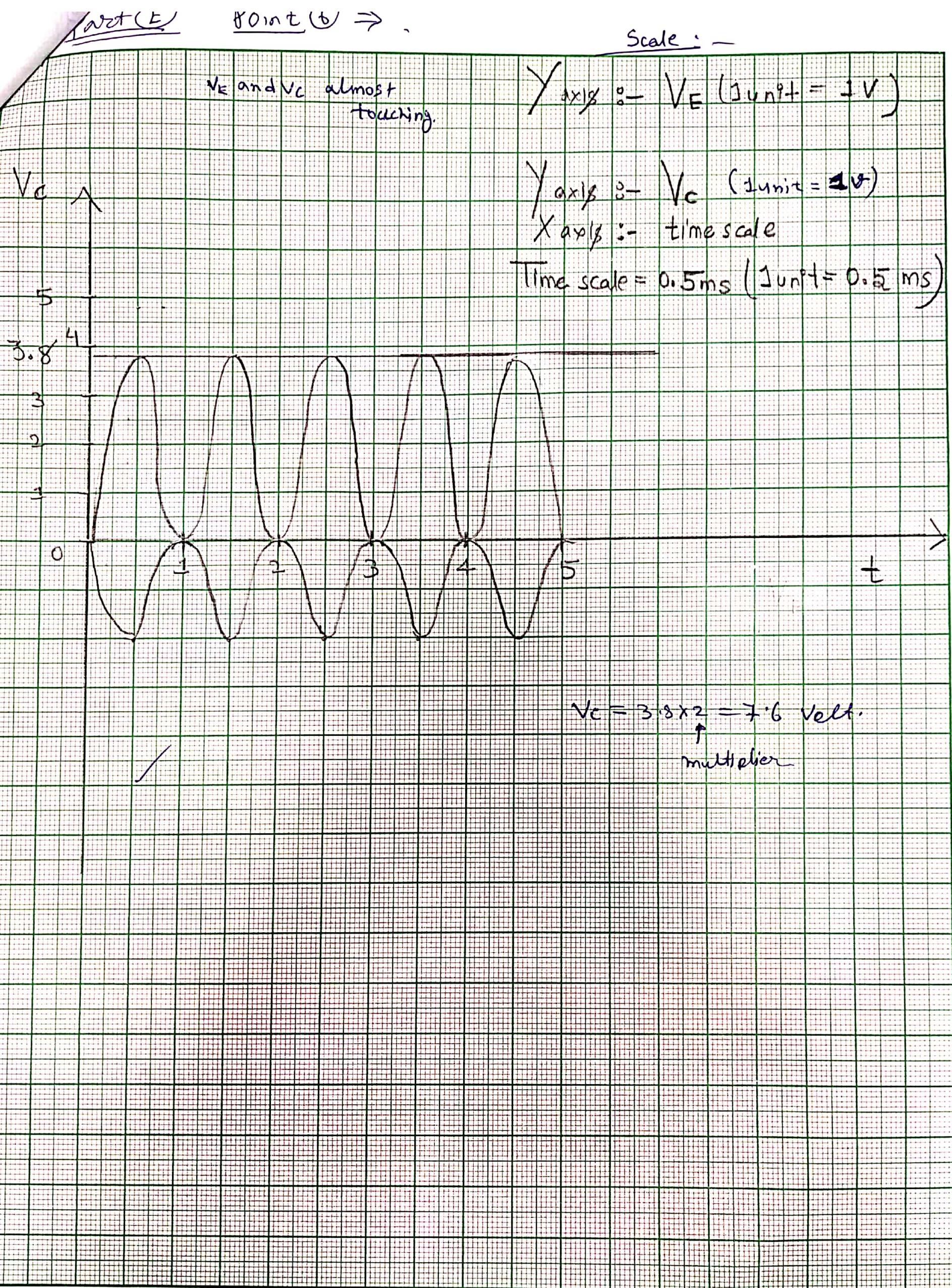

$$1). \quad V_E = 1.278V$$

$$V_C = 5.93V$$

$$V_{CC} = 11.95V$$

$$V_B = 1.916V$$

$$\therefore V_E < V_C < V_{CC}$$

In case of active region of a transistor (n-p-n),  $I_C$  should be moving into the transistor. For this to happen:-

$$V_{CC} > V_C \quad \& \quad V_C > V_E ; \quad V_B > V_E ;$$

$$\therefore V_{CC} > V_C > V_E$$

2)

Experimental

$$V_C$$

$$5.93V$$

$$V_E$$

$$1.278V$$

$$V_B$$

$$1.916V$$

$$V_{CC}$$

$$11.95V$$

Theoretical

$$\cancel{5.93}$$
  
$$4.91V$$

$$1.514V$$

$$2.164V$$

$$12V$$

$$I_E \quad 2.812mA \quad 3.221mA$$

$$I_C \quad 2.839mA \quad 3.222mA$$

$$I_B \quad 0.013mA \quad 0.014mA$$

$$\textcircled{3} \quad \beta_{\text{experimental}} = \frac{I_C}{I_B} = \cancel{27.83} \quad 218.38$$

$$\beta_{\text{theoretical}} = 200,$$

$$\textcircled{4} \quad \text{Part A: } A_v = -240.75$$

$$\text{Part B: } A_v = -117.64$$

Theoretical value :-

$$\text{In Pre-lab work: } A_v = -283.448,$$

\textcircled{5} Through MUVS, we get to know about the active region of the amplifier i.e. below which voltage it follows a linear relationship.